
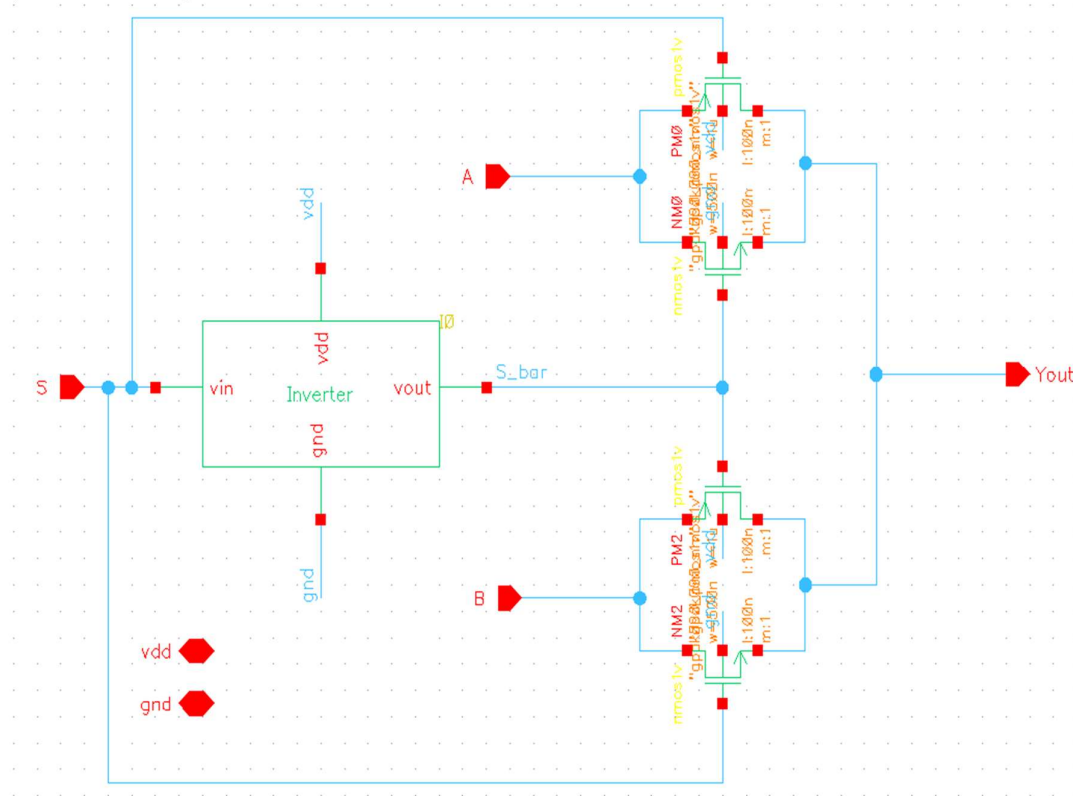


2:1 multiplexer using transmission gates.

A) Circuit Diagram:

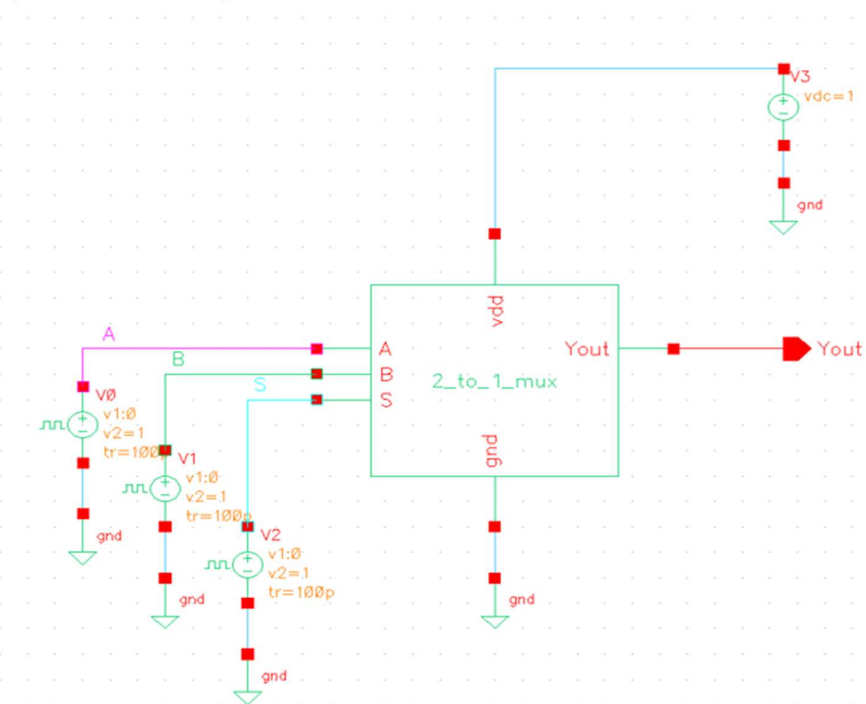

B) Testbench Diagram:



Transient response of 2:1 Multiplexer:

