
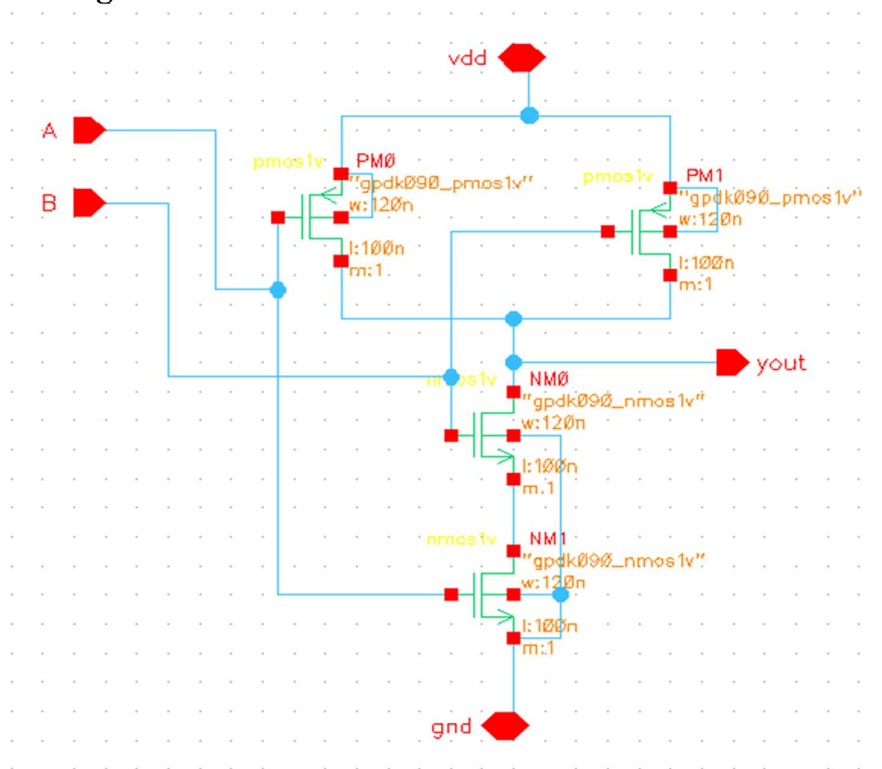



NAND gate schematic:

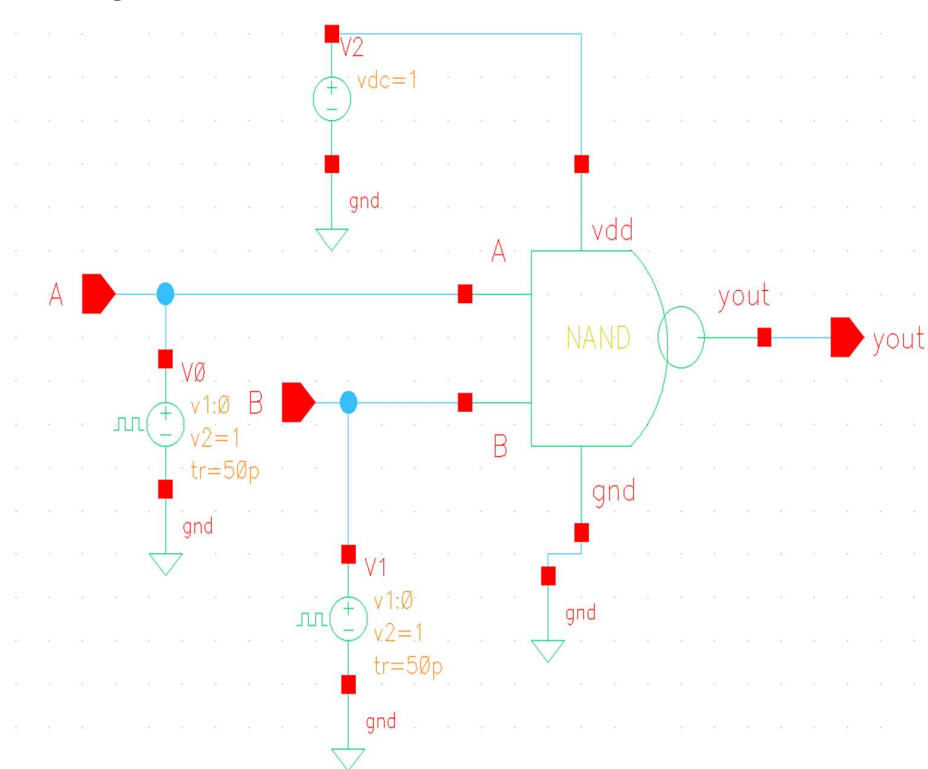

NAND gate testbench:



Transient response of NAND gate:

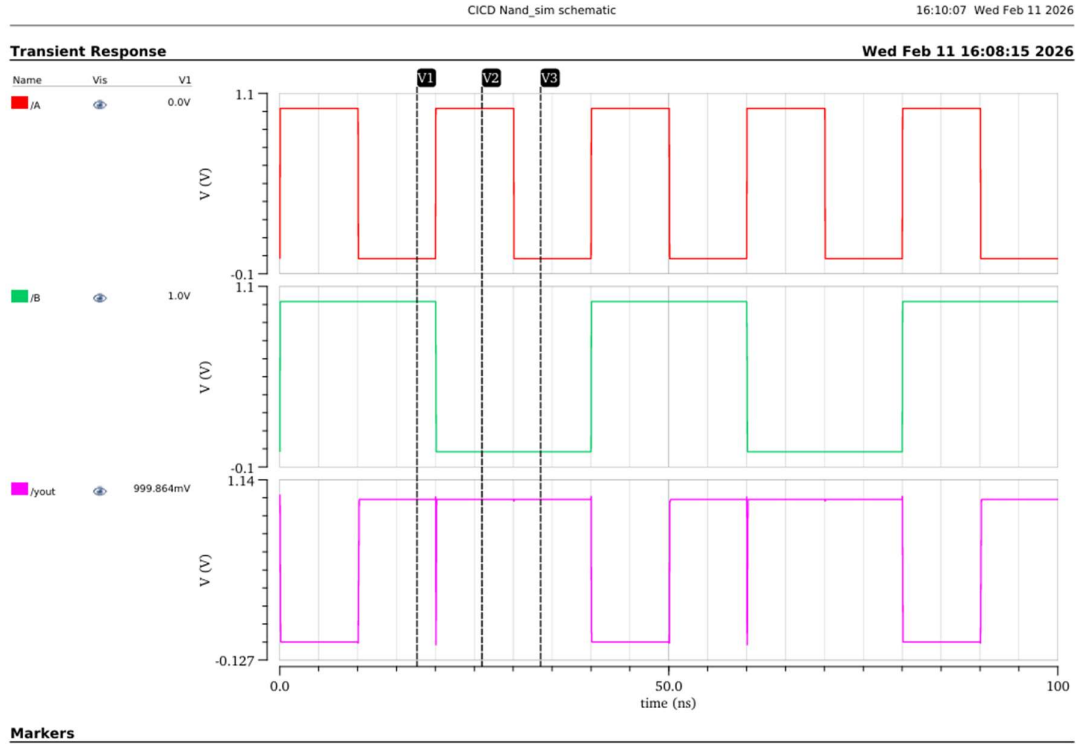

Layout Diagrams of NAND gate:

