
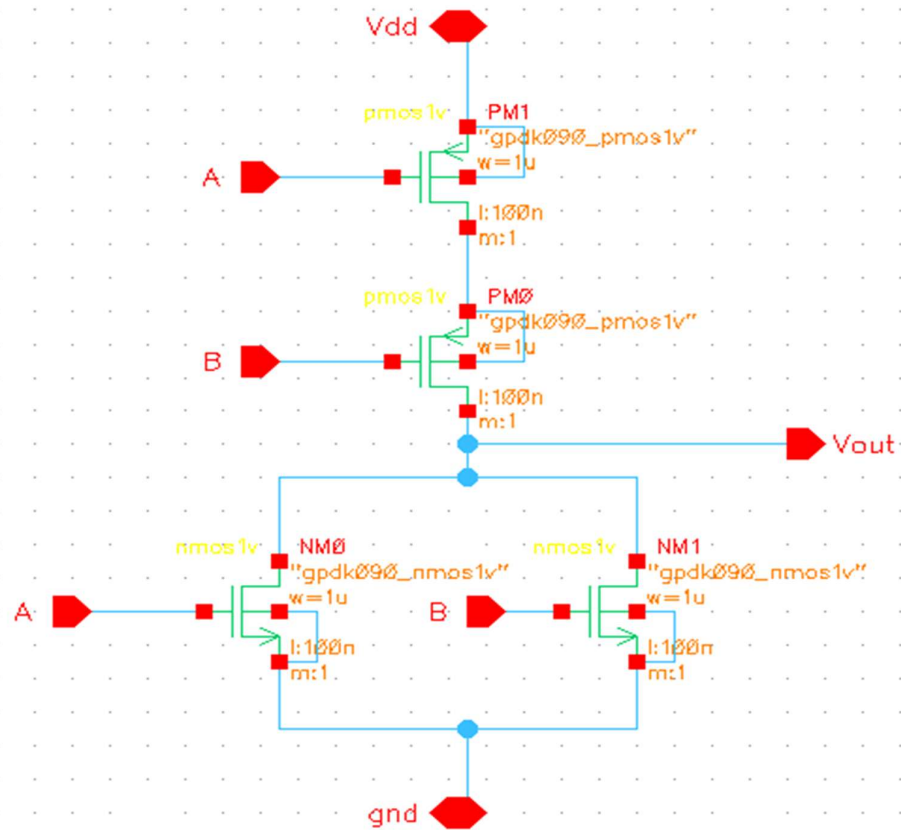



NOR gate schematic:

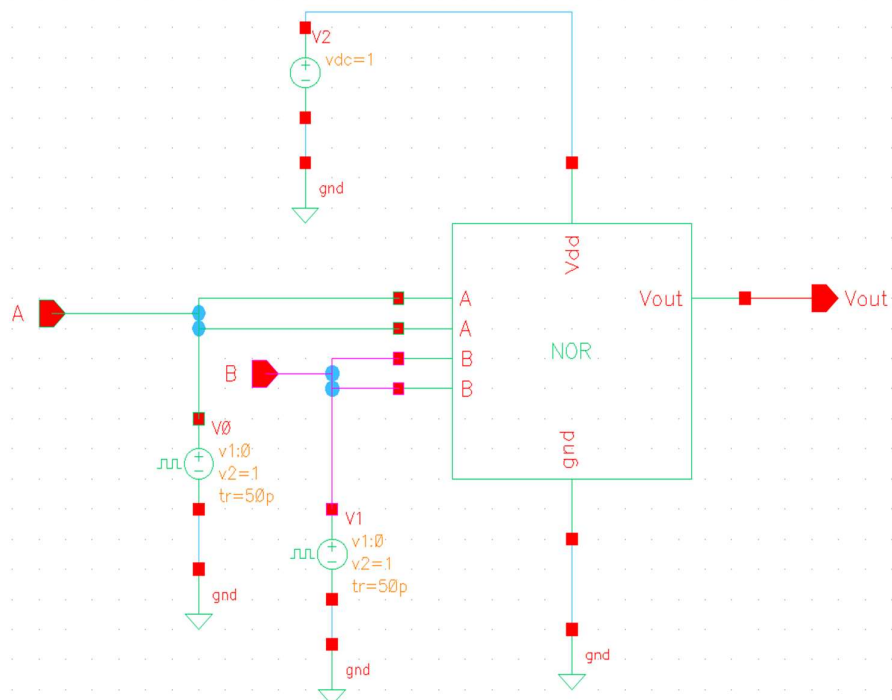

NOR gate testbench:



Transient response of NOR gate:

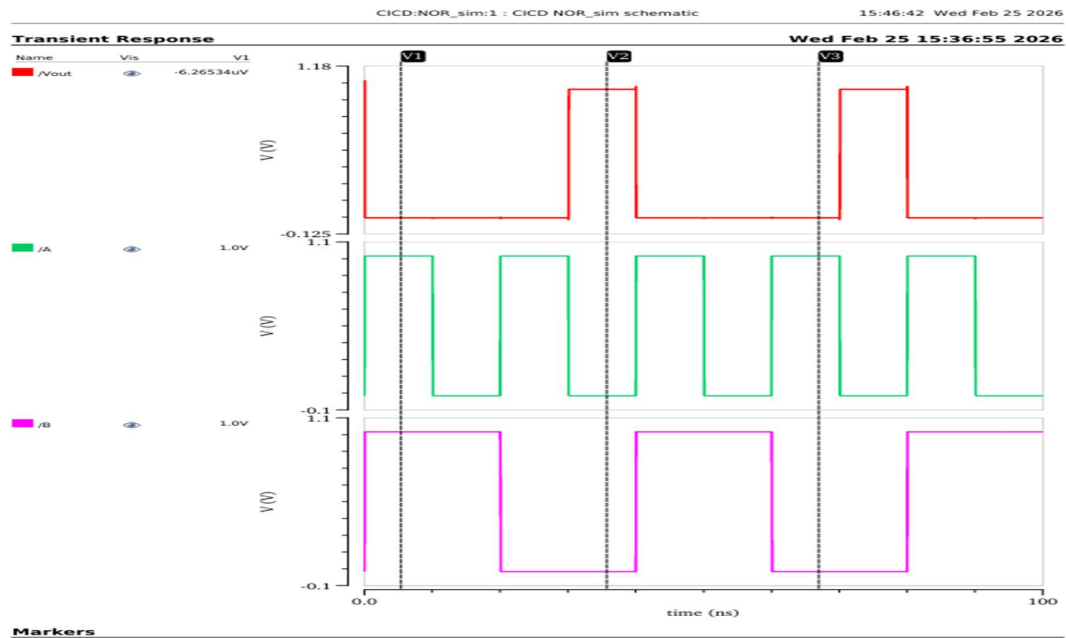

Layout Diagrams of NOR gate:

