

Layout of 2:1 multiplexer using transmission gates.

Specifications:

Technology: 90 nm

Supply voltage: 1.0V



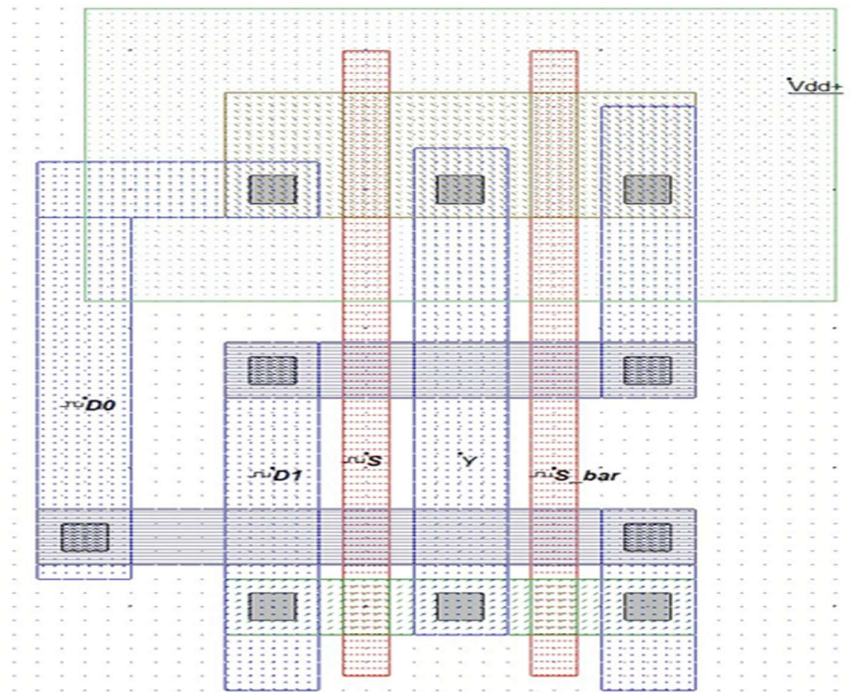


Diagram Screenshot:

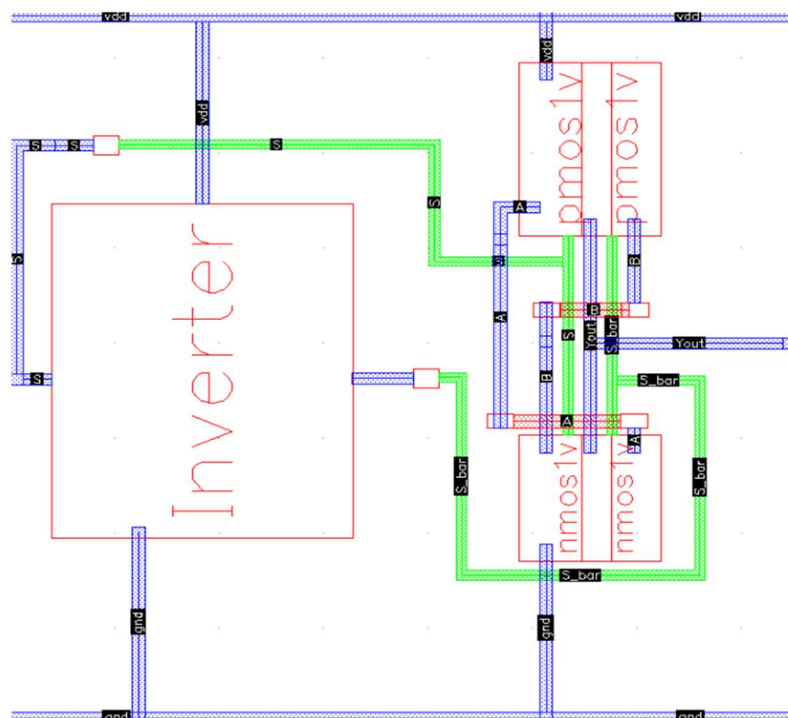


D flip-flop


A) Circuit schematic:

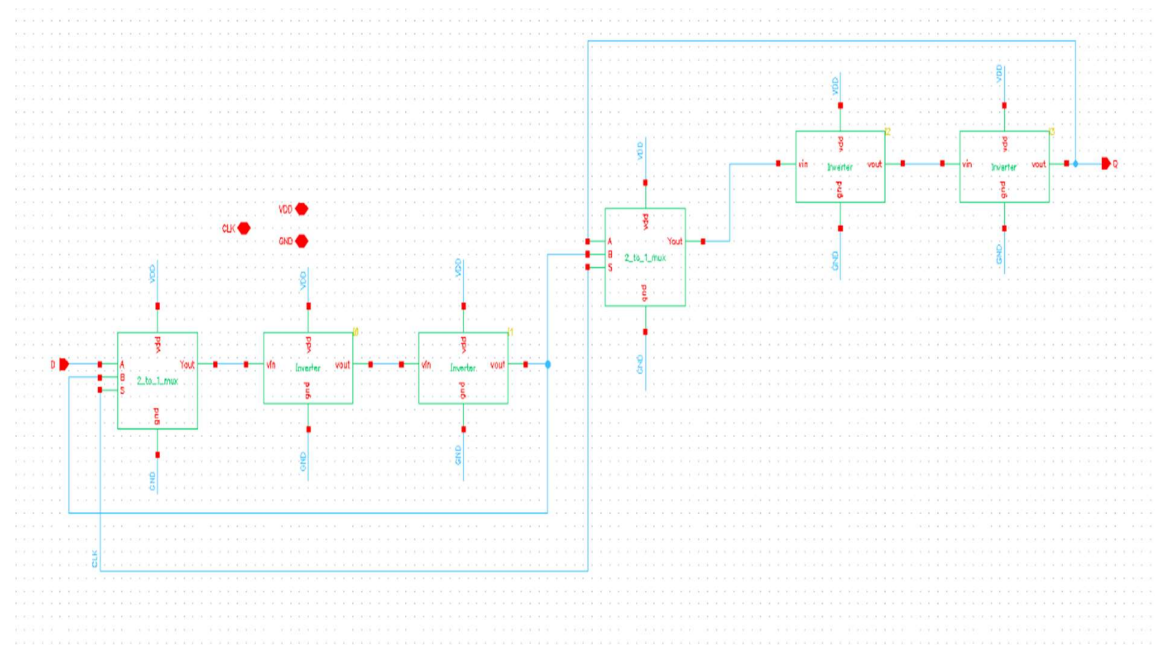

B) Testbench schematic:

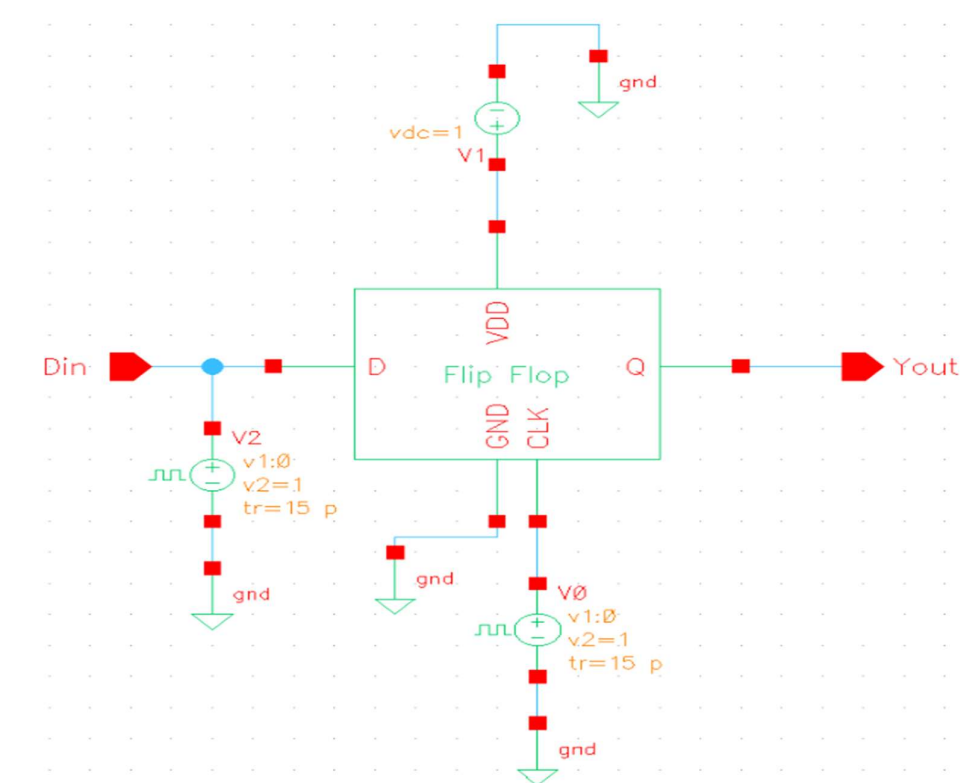

Transient Response:

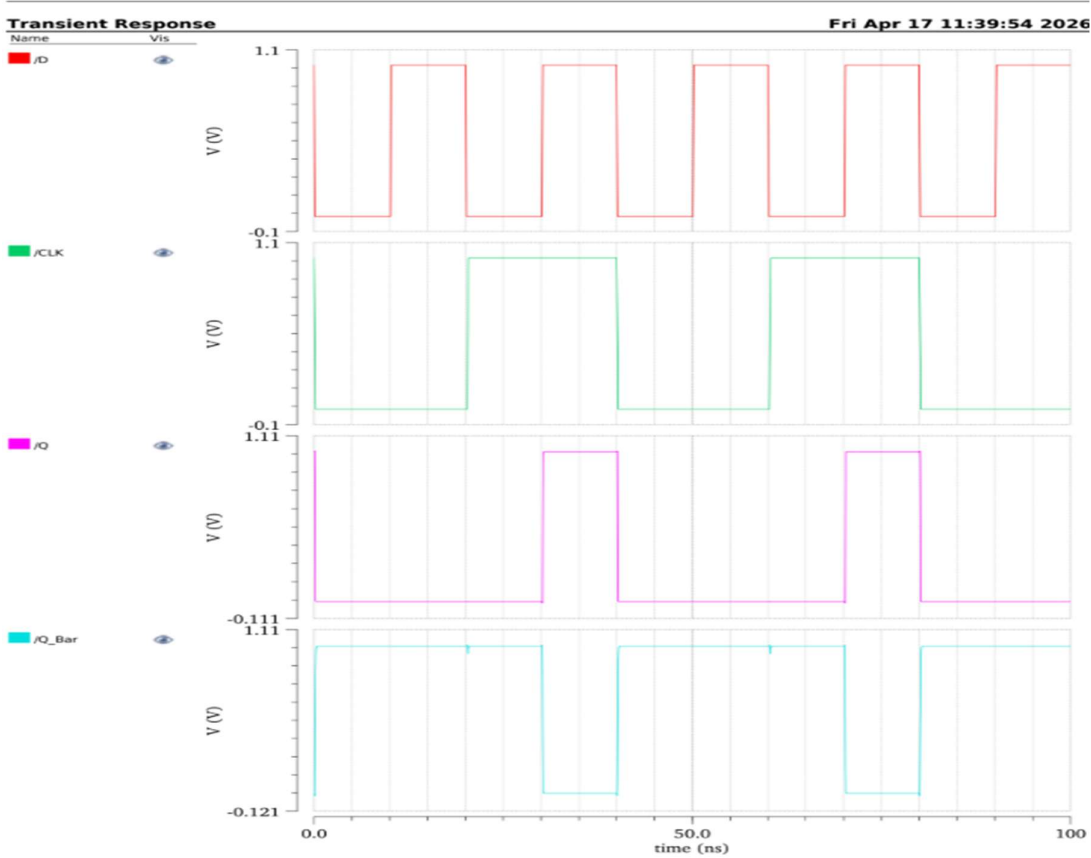

layout of D flip-flop.

Specifications:

Technology: 90 nm
Supply voltage: 1.0V

Layout Diagram:

