
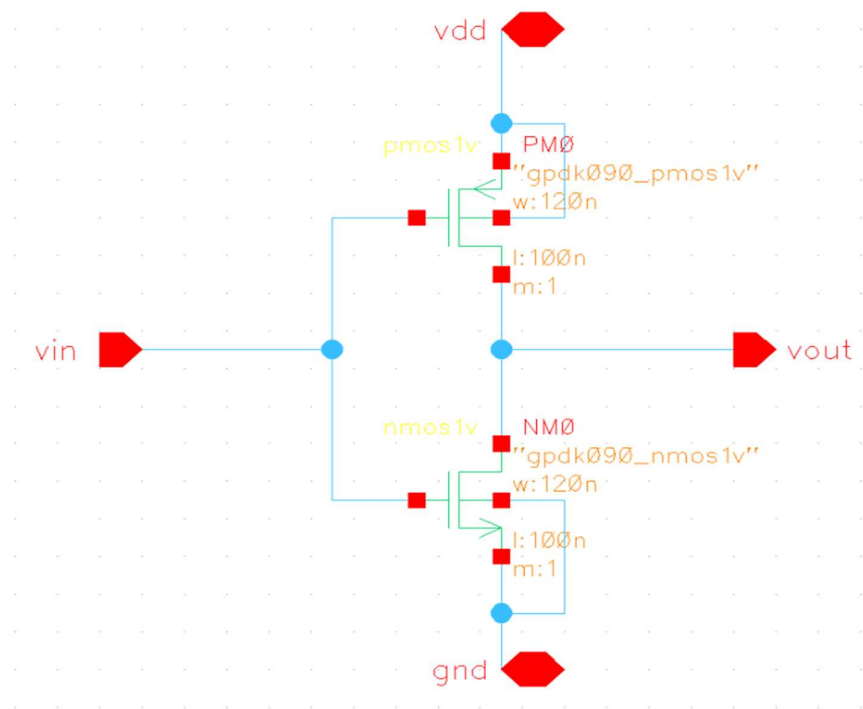


CMOS Inverter :


A) Circuit schematic:

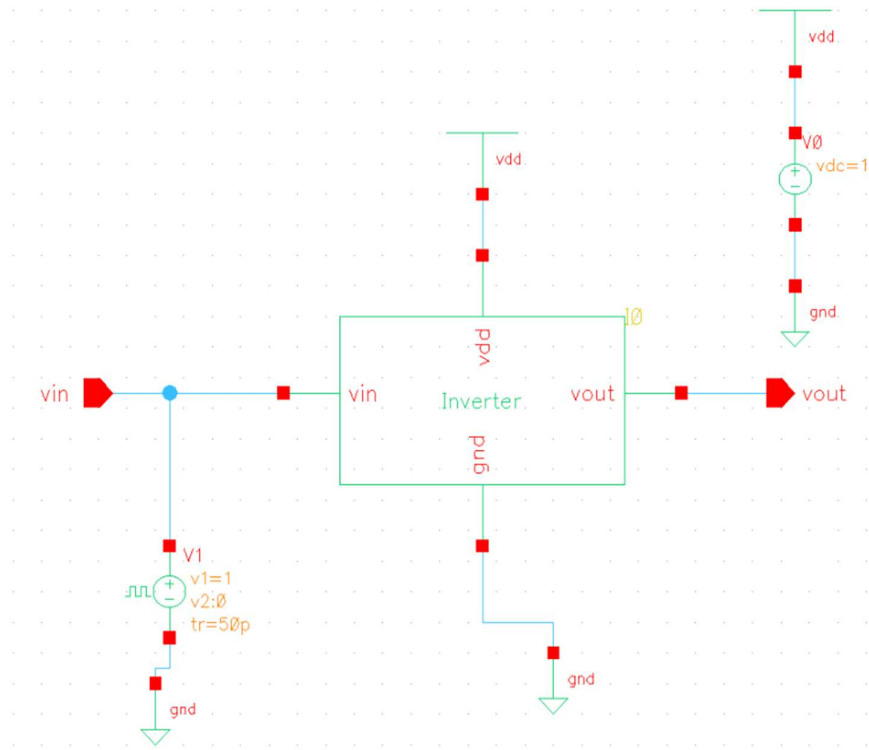


B) Testbench schematic:



A) Transient response:

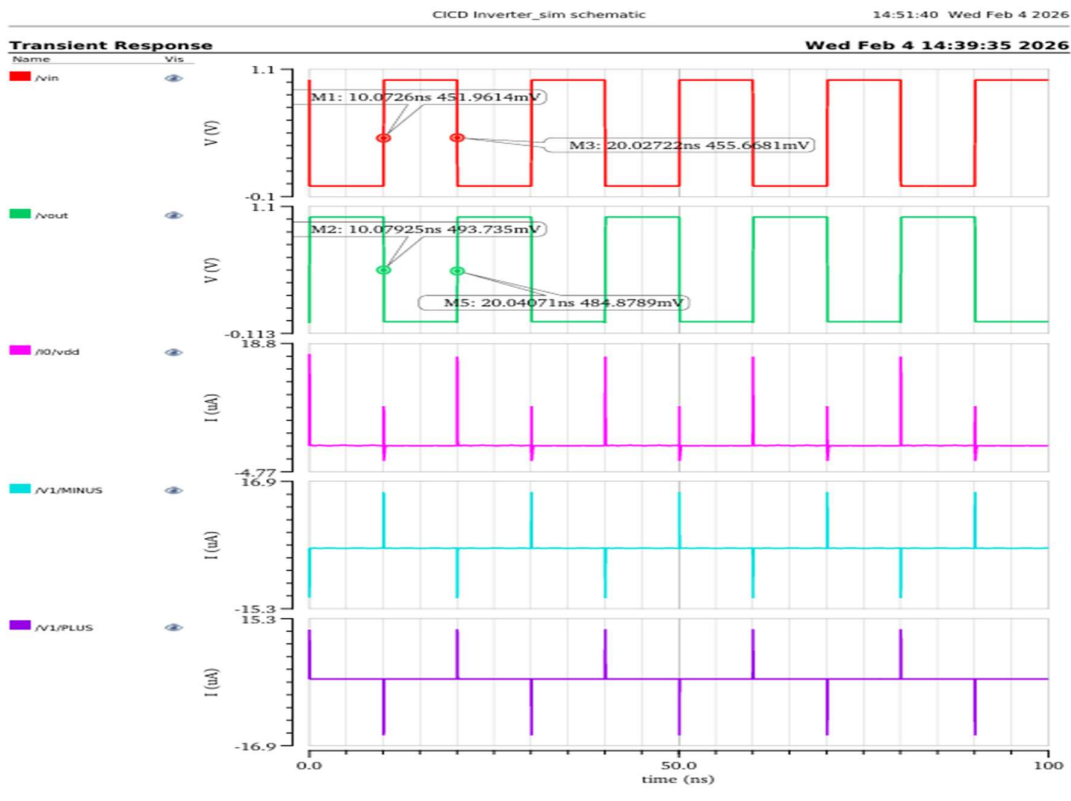

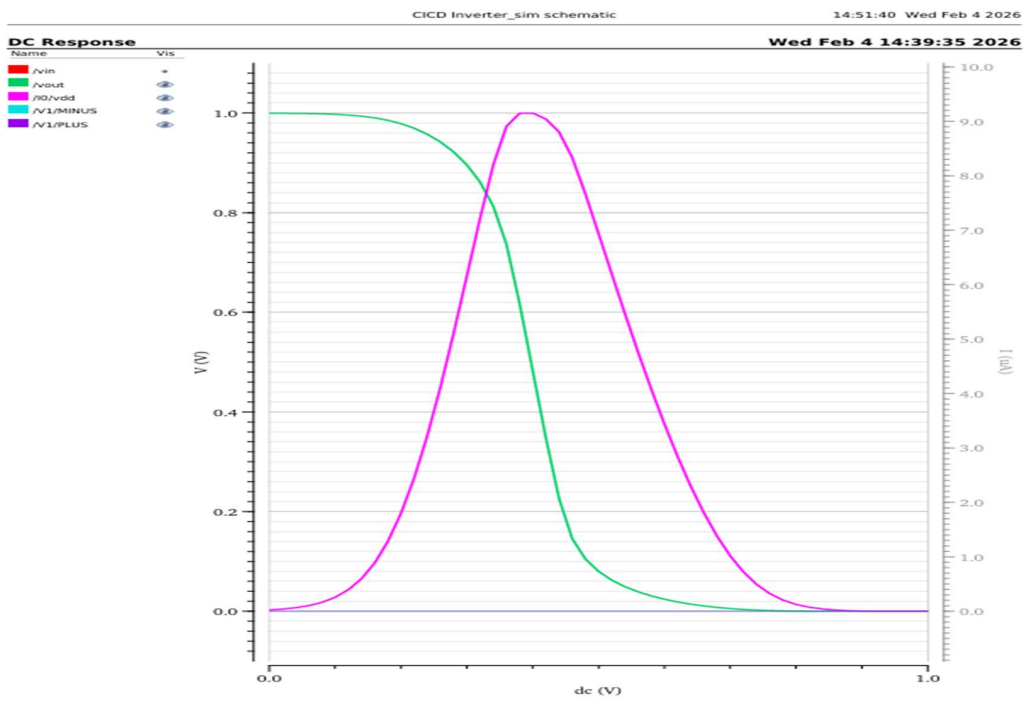B) Voltage transfer characteristics (DC response):



CMOS Inverter layout

